

WIRELESS IR HEADPHONE RECEIVER

Contributed by Y.Kwon
Monday, 21 April 2008

IR detector diode D1 intercepts the IR signal at around 40 kHz and feeds it from U1, a high-gain preamp, to PLL, U2, a 4046 configured to serve as an FM detector. U3 is an audio amplifier that feeds a pair of headphones or a speaker.

Schematic Circuit