

HOME SECURITY SYSTEM

Contributed by Y.Kwon
Friday, 09 May 2008
Last Updated Friday, 09 May 2008

This alarm circuit activates when S1 through S5 are activated. This lights LED1 and activates Q1 via IC1C and IC1D. RY1 is wired to self latch. S10 is used to reset. When key switch S1 is activated or when re-entry buttons at S6 are depressed, IC1C is deactivated until RC network R7/C3 charges. Schematic