

GENERAL-PURPOSE PREAMPLIFIER

Contributed by Y.Kwon
Monday, 12 May 2008
Last Updated Monday, 12 May 2008

Suitable for general audio use, the preamp circuit uses a feedback pair. Current gain is set by the ratio of $(R4+R6)/R4$. Schematic of General-Purpose Preamplifier