

WIDEBAND TWO-POLE HIGH-PASS FILTER

Contributed by Y.Kwon
Monday, 12 May 2008
Last Updated Monday, 12 May 2008

The circuit provides a 10MHz cutoff frequency. Resistor R3 ensures that the input capacitance of the amplifier does not interact with the filter response at the frequency of interest. An equivalent low pass filter is similarly obtained by capacitance and resistance transformation. Schematic of Wideband Two-Pole High-Pass Filter